

CSC258 lab4

Part1:

3. Test vector does not work, because this is sequential circuit.
4. Should change the clk to 1, otherwise value of D will not be sent to the output.

Part2:

2. a. The output will be used as new input and the HE display keep changing.
- b. When clock goes high, the output will keep changing.
- c. 2n bit
- d. The most significant bit will be ignored, it will not change the shift register.

3. a.

status	B	A	S
pass	1111	0000	0000 1111
pass	1101	0010	0011 0100
pass	1111	1000	0000 1111
pass	1000	1111	0000 0000

b.


status	B	A	S
pass	1111	0000	0000 1111
pass	1111	0001	0000 0111
pass	1100	1000	0000 1100
pass	1100	0010	0000 0011

c.


status	A	B	S
pass	1101	0011	0000 0111
pass	1101	0001	0000 1101
pass	1101	0101	0000 0001

Part3

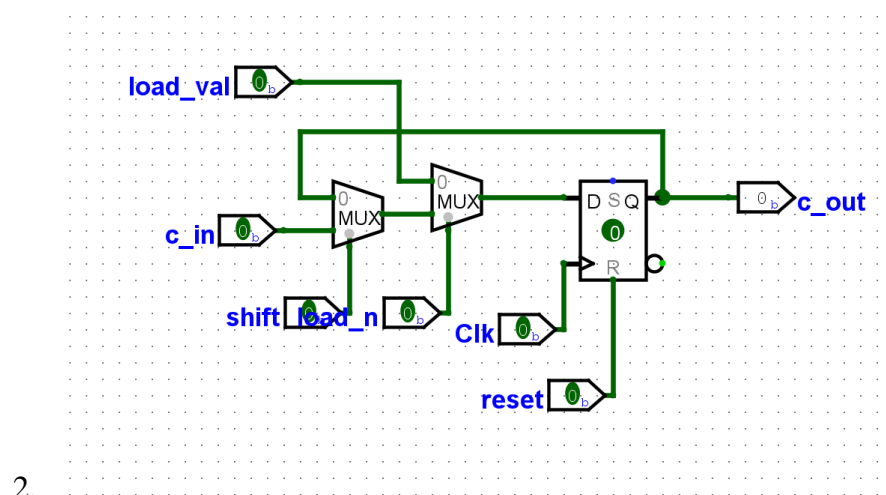
1. When load_n=0 and shift_right = 0, it will load the value.




3. Load value:

 

Shift right = 1, ASR=1:

 

Shift right = 1, ASR = 0:

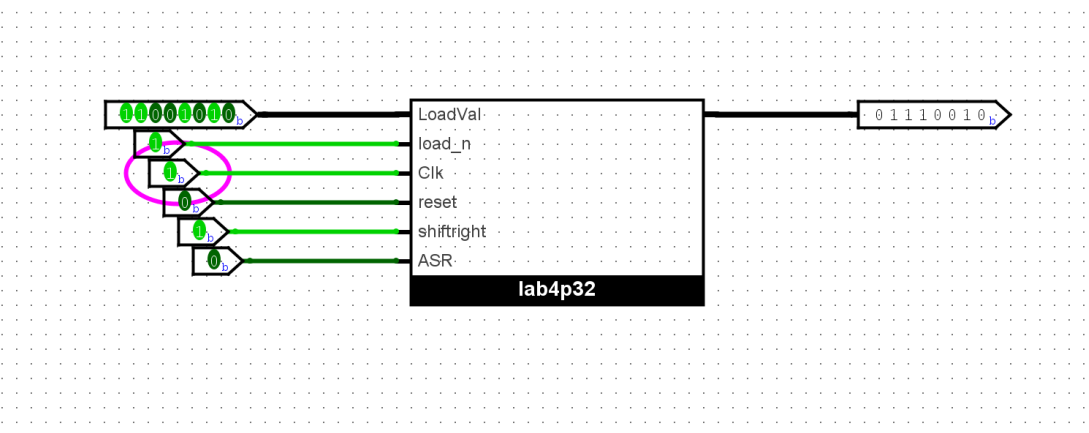

4. If we do not have reset, then we don't have output value in the D latch.